

CSCI 350 Digital Logic and Computer Organization
 G. Pothering
 Spring 2020
 Assignment 4 Due February 13, 2020

1. Implement a 16-1 multiplexer using **only** 4x1 multiplexers. $2^n = 4$ $n=2$ on bottom
2. Implement a 4 x16 decoder with enable using **only** three 3x8 decoders (again, with enable).
3. Use **only** an 8-1 multiplexer to implement the function $f(x,y,z) = \Pi(2,5,6)$. (see page 161 for an example)

The purpose of the rest part of the assignment is to familiarize you better with the notion of propagation delays for signals in a circuit and for you to see some of the tradeoffs that arise in circuit design because of attention to propagation delay. Remember, the *propagation delay* for a gate is the time it takes for a gate to (possibly) change its output value following a change in its input values.

time 4 gate 2 change output

4. Consider the full adder circuit in your textbook on page 165.
 - a. Assuming each of the logic gates used in this circuit has a propagation delay of 4 ns (nanoseconds), what are the delays for generating the sum and carry-out for this full adder?
 - b. Using the "ripple adder" approach described on page 165 to implement a 4-bit adder from four 1-bit adder, calculate the propagation delays for the sum and carry-out for this 4-bit adder.
5. In this exercise we are going to show how we can speed up the propagation delays for ripple adders.
 - a. Your textbook describes an alternate type of adder known as a **carry-select adder** on page 166. Show how you could implement a 2-bit adder from 1-bit adders using this approach and calculate the propagation times for the sum and final carry-out.
 - b. Now use carry-select to design a 4-bit adder from 2 bit adders that were themselves designed by carry-select. Calculate the propagation times for the sum and final carry-out for this 4-bit adder.
6. The approach described in problem 14 on pages 238-39 of your textbook implements what is known as a carry-look-ahead adder. Use carry-look-ahead to implement a 4-bit adder from four 1-bit adders and calculate the propagation times for the sum and final carry-out for this 4-bit adder.

8 input


Assignment 4

Shetali E


#1 Implement a 16-1 Mux using 4x1 Mux's

$$2^n = 4 \quad \Delta$$



$$n = 2$$

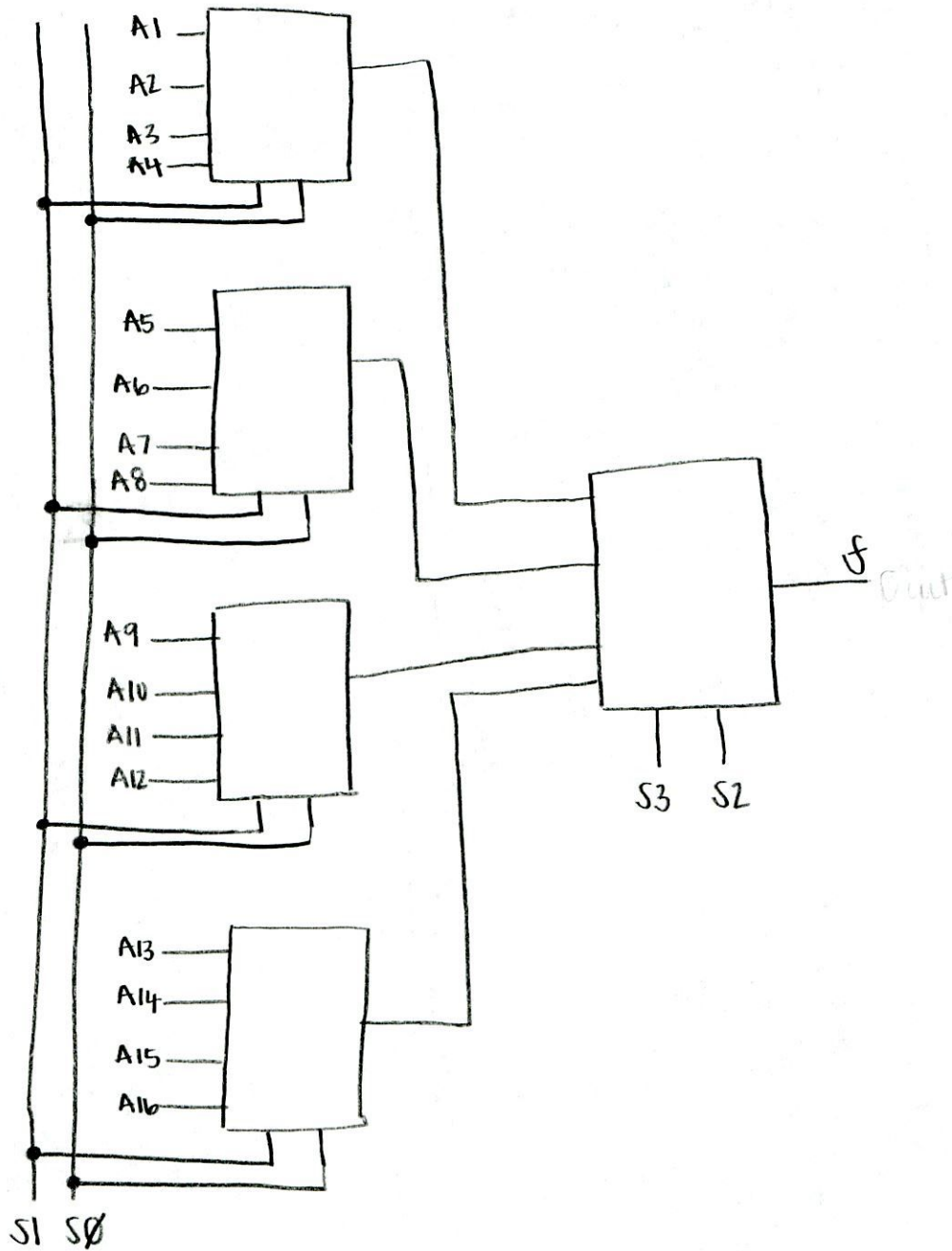
 
#2 4x16 decoder w/ enable using 3x8 decoders


  
#3) 8-1 Mux to implement $f(x,y,z) = \prod(2,5,6)$
 where it is \emptyset



(a) Sum Delays = $4 + 4 = 8$ nano second delay


Carry Out Delay = $4 + 4 + 4 + 4 = 16$ nano second delay

4b) Ripple Adder (4 bit)

$$\text{Sum Delay} = \underbrace{\boxed{8} + \boxed{16}}_1 + \underbrace{\boxed{8} + \boxed{16}}_2 + \underbrace{\boxed{8} + \boxed{16}}_3 + \underbrace{\boxed{8}}_4 = 80 \text{ nano seconds}$$

$$\text{Carry out Delay} = \underbrace{\boxed{16}}_1 + \underbrace{\boxed{16}}_2 + \underbrace{\boxed{16}}_3 + \underbrace{\boxed{16}}_4 = 64 \text{ nano seconds}$$

5a) Carry Select Adder

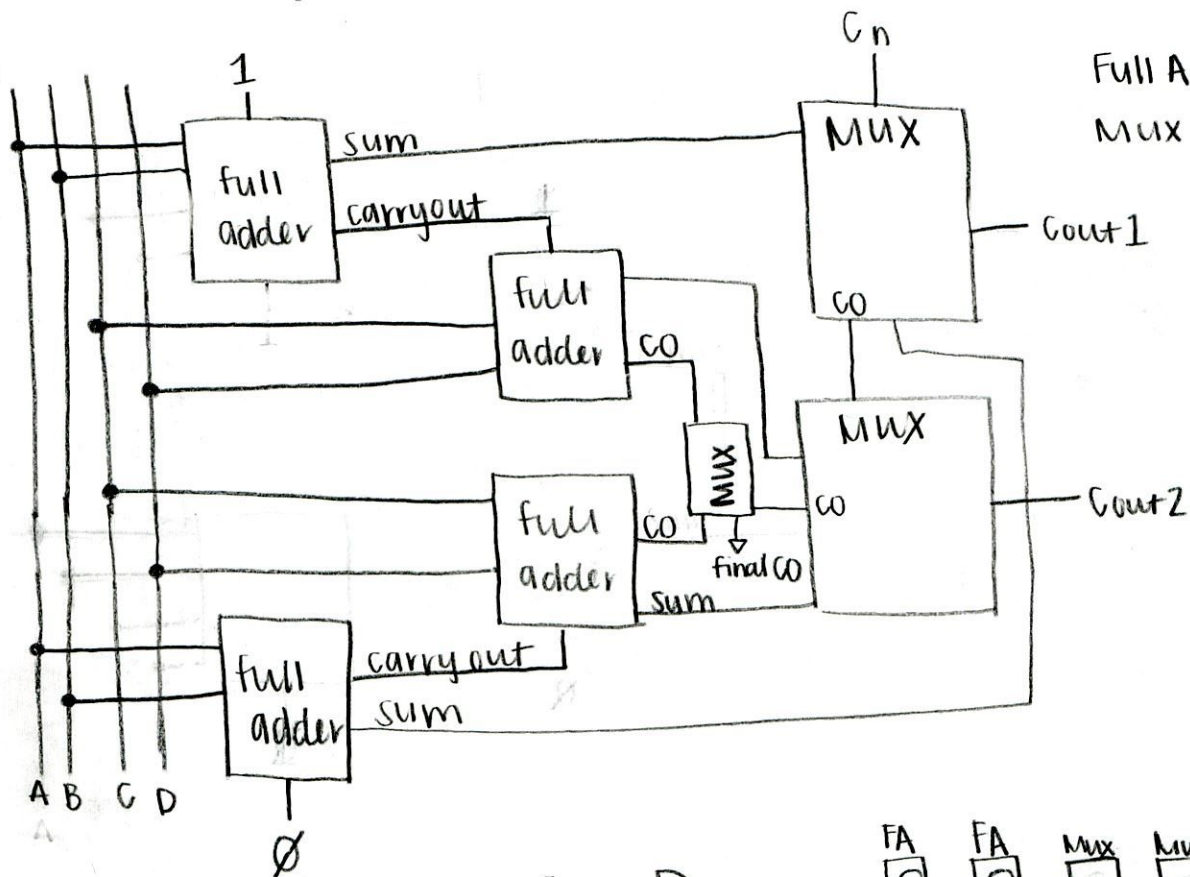

$$\text{Sum Delay} = \boxed{8} + \boxed{8} + \boxed{12} + \boxed{12} = 40 \text{ nanoseconds}$$

$$\text{Final Carry Out Delay} = \underbrace{16 + 16 + 12 + 12}_{\text{last Mux}} + \boxed{12} = 68 \text{ nanoseconds}$$

5b

do we need to draw?

$$\text{Sum delay} = \underbrace{40}_{2 \text{ Full Adders}} + \underbrace{40}_{2 \text{ FA}} + \underbrace{12}_{\text{Mux}} + \underbrace{12}_{\text{Mux}} = 104 \text{ nano sec}$$




Stay the same time no matter the # of inputs

Carry out

$$\text{delay} = 68 + 68 + 12 + 12 + 12 = 172 \text{ nanosec}$$

(b) Carry look-ahead adder

 

calculate 1 + carry bit before sum = $\frac{1}{\text{wait time}}$
will 1 appear in prev value?

\therefore use Cin

Sum delay =

$$\left(\underbrace{3}_{\text{gates w/*}} \times \underbrace{4}_{\text{Sec}} \right) + \underbrace{8}_{\text{last FA}} = 20 \text{ nano Seconds}$$

Carryout delay =

$$\underbrace{3}_{\text{gates}} \times \underbrace{4}_{\text{Sec}} + \underbrace{16}_{\text{last FA}} = 28 \text{ nano Seconds}$$

test if any
before produced
a count of 1

$$\begin{array}{r}
 \begin{array}{cc}
 A_1 & A_0 \\
 B_1 & B_0
 \end{array} \\
 \hline
 \text{Cin} & S_0
 \end{array}
 \quad \begin{array}{l}
 \text{Carry in} \\
 \text{Carry out}
 \end{array}$$

$$S_1 = C_0 \oplus (A_0 + B_0)$$

$$C_1 = A_1 B_1 + B_1 C_0$$

$$C_0 = A_0 B_0 + B_0 \text{Cin}$$